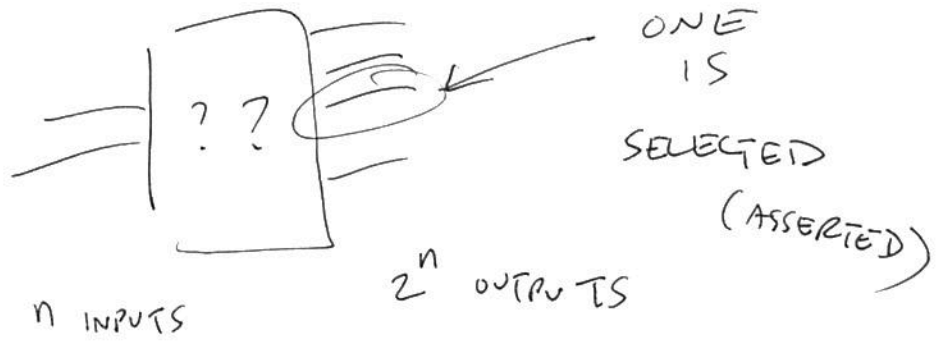



THE DECODER



How?


1-2 LINE DEC.

I_0	I_1	O_0
0	1	0
0	0	1
1	0	0
1	1	1

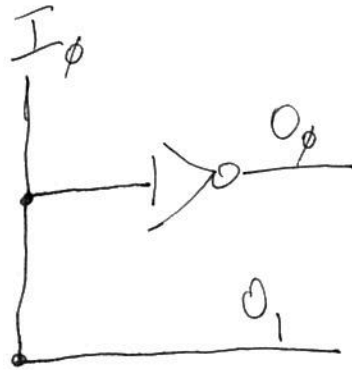


3-8 DECODER

I_0	I_1	I_2	O_0	O_1	O_2	O_3	O_4	O_5	O_6	O_7
0	0	0	1							
0	0	1		1						
0	1	0			1					
0	1	1				1				
1	0	0					1			
1	0	1						1		
1	1	0							1	
1	1	1								1

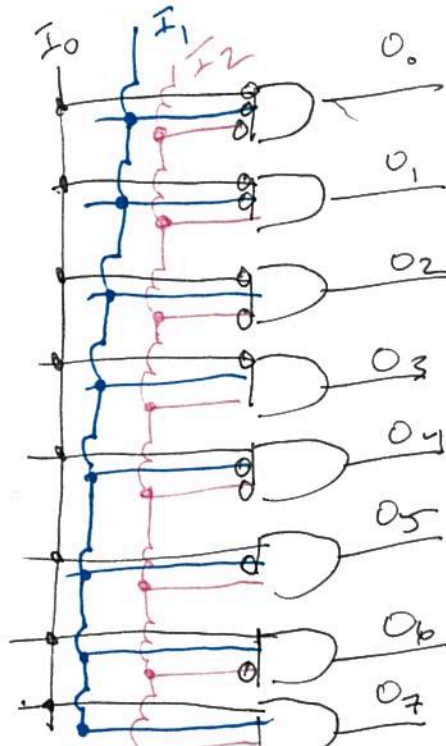

THE ENCODER

"SELECT A LINE"

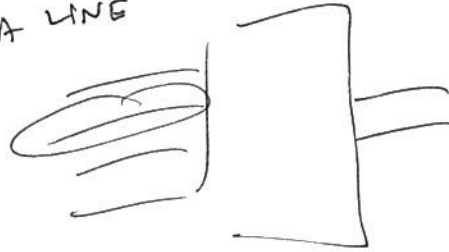


2^n INPUTS

n OUTPUTS


"GIVE ME ITS ADDRESS AS A BINARY #"

How? 4-2 ENCODER


I_0	I_1	I_2	I_3	O_0	O_1
1	0	0	0	0	0
0	1	0	0	0	1
→ 0	0	1	0	1	0
→ 0	0	0	1	1	1
↓	↓	↓	↓		
A	B	C	D		

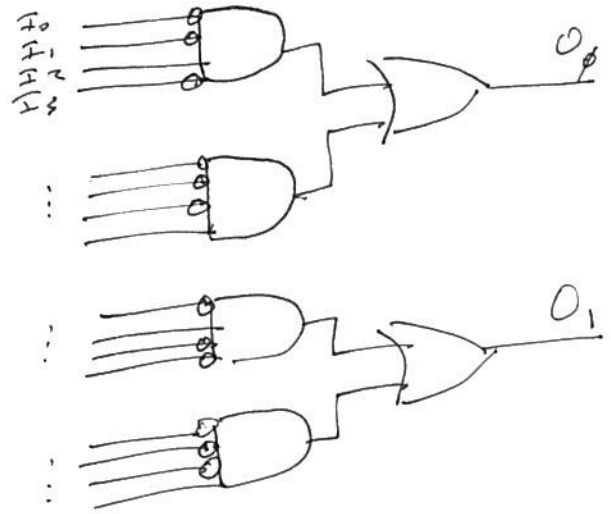


THE MULTIPLEXER

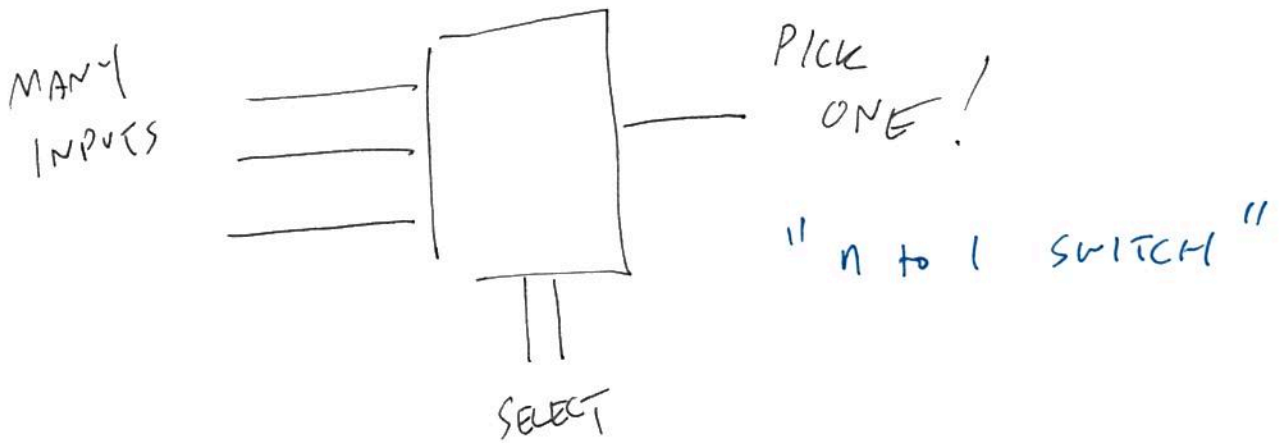

2 INPUTS

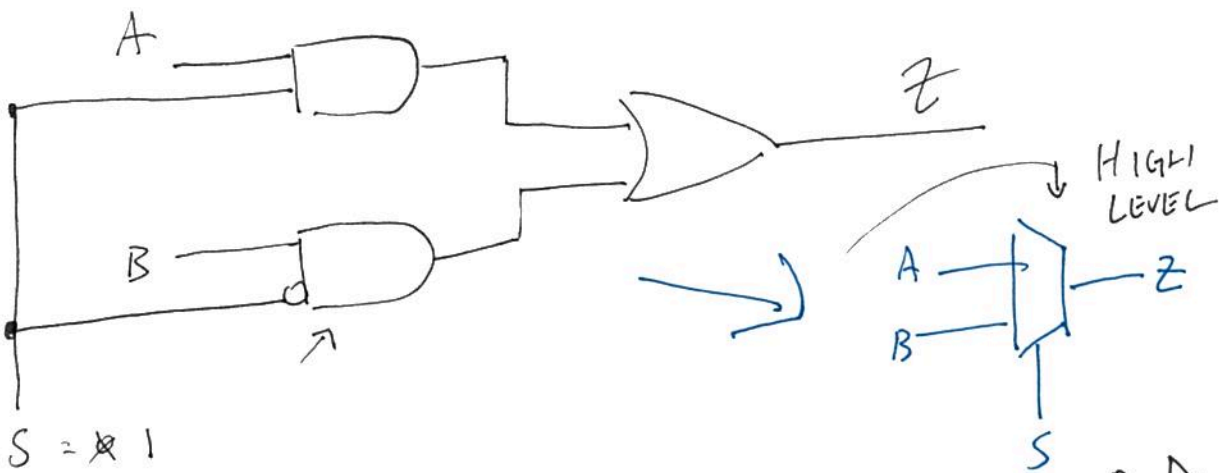

4 INPUTS


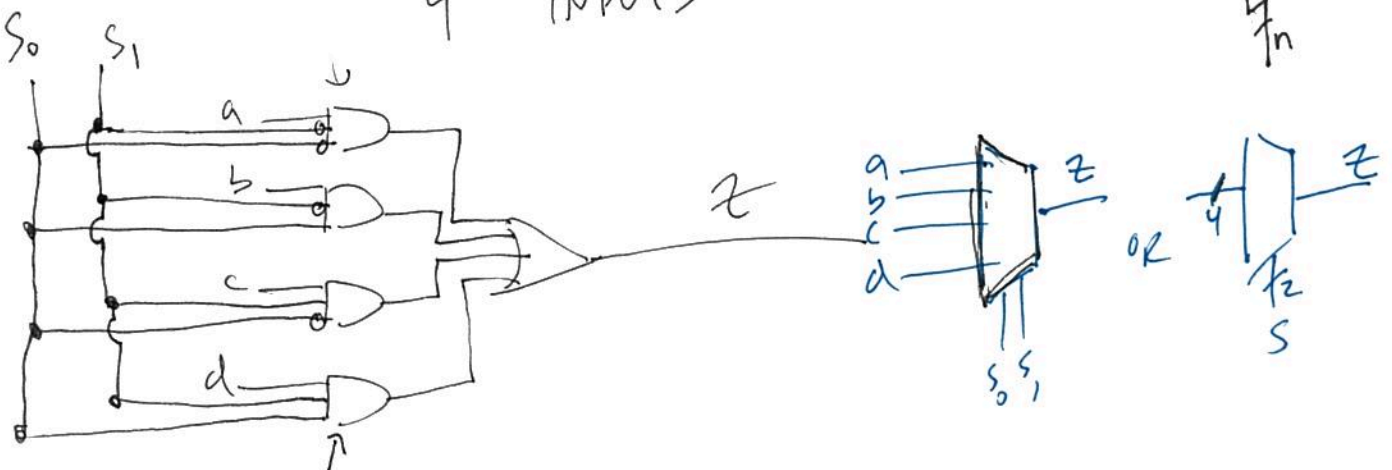


CALCULATOR

4 FUNCTIONS

- BITWISE AND (A, B)
- BITWISE OR (A, B)
- BITWISE XOR (A, B)
- BITWISE NOT (A)

WE ALREADY HAVE COMPONENTS!

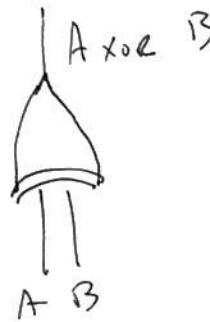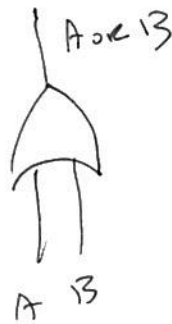

WE NEED TO SELECT ONE BASED ON A NUMBER "OPCODE"

00 MEANS "AND"


01 MEANS "OR"

10 MEANS "XOR"

11 MEANS "NOT"

(ALL IT
S[1:0])

???

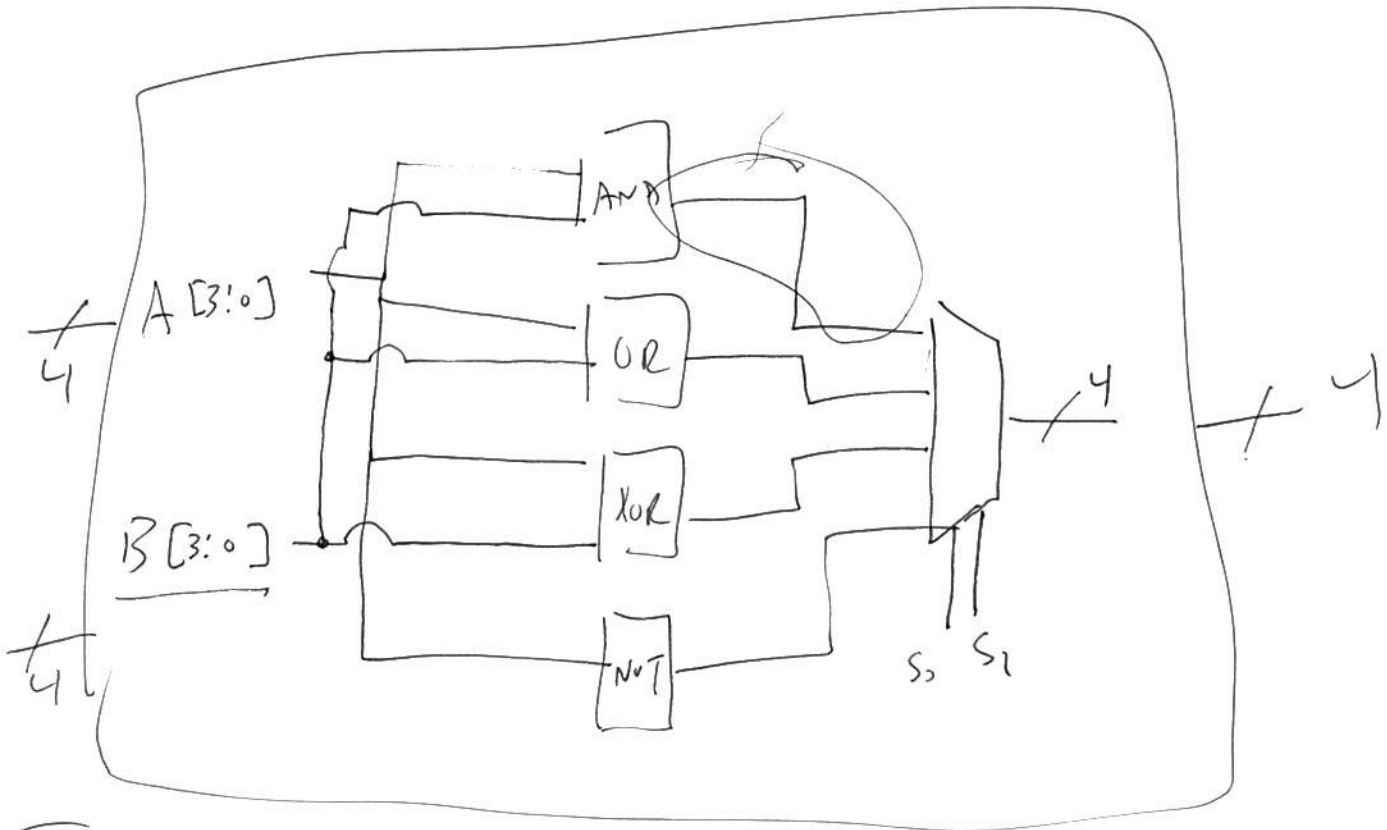


I

ALU




0

S ₀	S ₁	
0	0	AND
0	1	OR
1	0	XOR
1	1	NOT

FLIPPING BITS

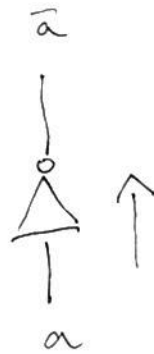

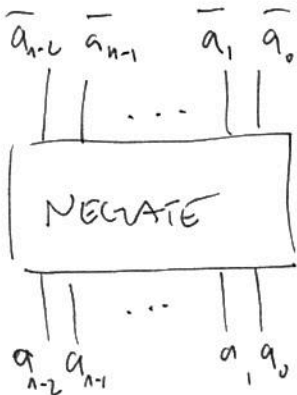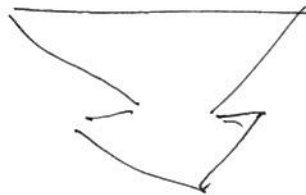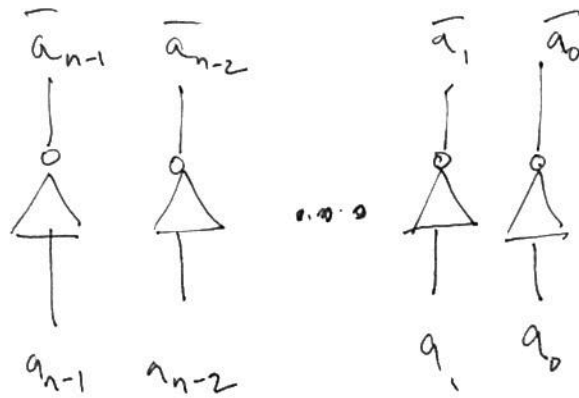
$$A = \{a_{n-1}, a_{n-2}, \dots, a_1, a_0\}$$






OR




OR

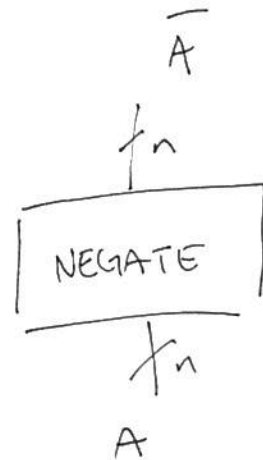

BITWISE OPS

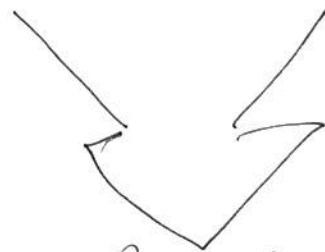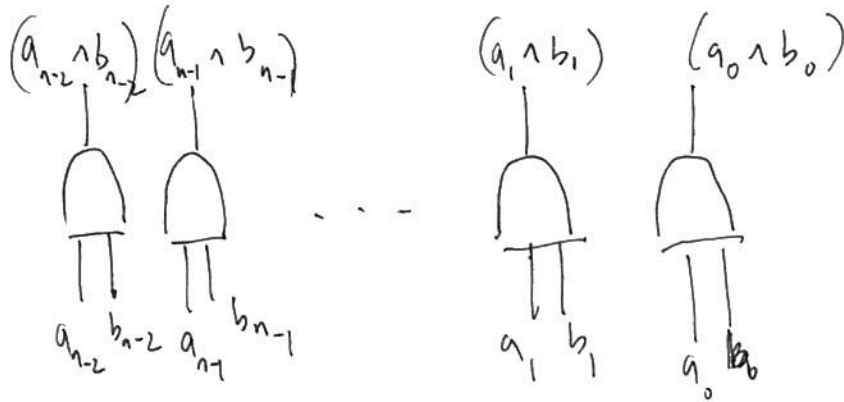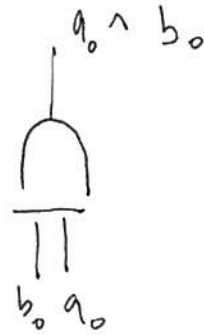

$C (A \wedge B)$
 f_n

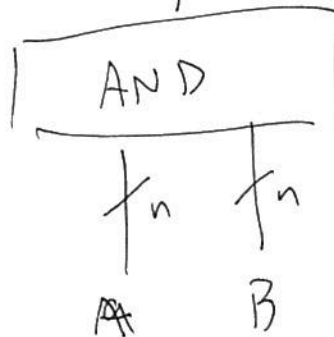

SAME FOR

- OR
- XOR
- NAND
- NOR
- VARIABLE

THE FULL ADDER

How To ADD 2 BINARY #'s?

MAKE A TRUTH TABLE!

INPUTS : A B ... C_{IN}




OUTPUTS : S ... C_{OUT}

C_{IN} C_{OUT}
 $\begin{array}{r} 101 \\ + 01 \\ \hline 0 \end{array}$ ←

A	B	C_{IN}	S	C_{OUT}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	↓	↓

$$S = \bar{A}\bar{B}C_{IN} + \bar{A}B\bar{C}_{IN} + A\bar{B}\bar{C}_{IN} + ABC_{IN}$$
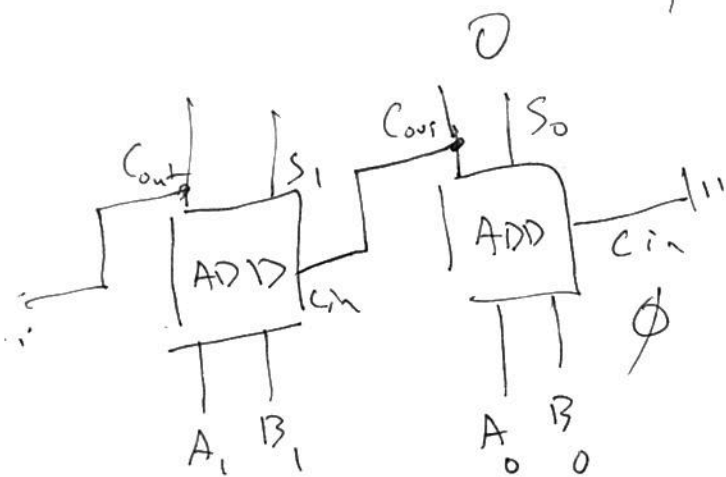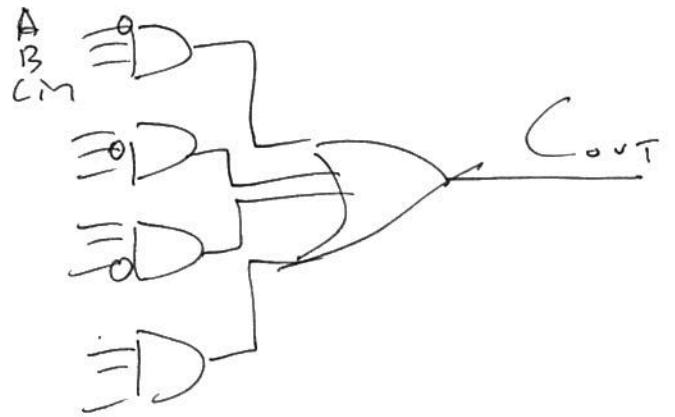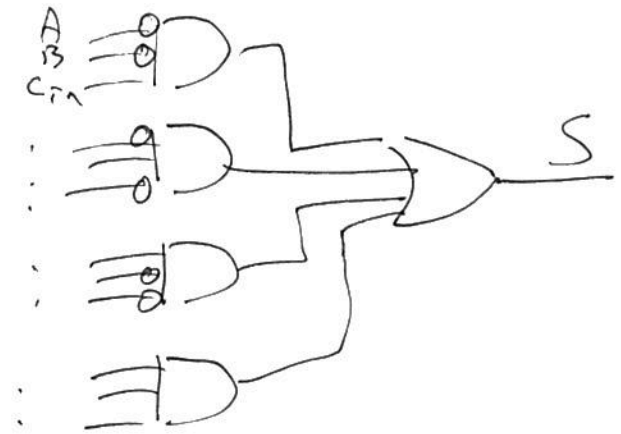
$$C_{OUT} = \bar{A}BC_{IN} + A\bar{B}C_{IN} + A\bar{B}\bar{C}_{IN} + ABC_{IN}$$



1-bit ADDER
"FULL ADDER"

